


# DIGITAL DESIGN

Lecture 16

Sarang Dhongdi
 
## BCD to 7-Segment decoder

- Design a logic that will convert a NBCD value to 7-segment equivalent.



A	B	C	D	a	b	c	d	e	f	g
0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	1	0	0	1	1	1	1
0	0	1	0	0	0	1	0	0	1	0
0	0	1	1	0	0	0	0	1	1	0
0	1	0	0	1	0	0	1	1	0	0
0	1	0	1	0	1	0	0	1	0	0
0	1	1	0	1	1	0	0	0	0	0
0	1	1	1	0	0	0	1	1	1	1
1	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	1	1	0	0

## Functions


- $a = \Sigma (1,4,6)$
- $b = \Sigma (5,6)$
- $c = \Sigma (2)$
- $d = \Sigma (1,4,7,9)$
- $e = \Sigma (1,3,4,5,7,9)$
- $f = \Sigma (1,2,3,7)$
- $g = \Sigma (0,1,7)$

AB \ CD	00	01	11	10
00		1		
01	1			1
11	X	X	X	X
10			X	X


AB \ CD	00	01	11	10
00		1		
01	1			1
11	X	X	X	X
10			X	X

Handwritten annotations:  $A'B'C'D$  above the 01 column, and  $BD'$  next to the 10 column.

## IC 7447

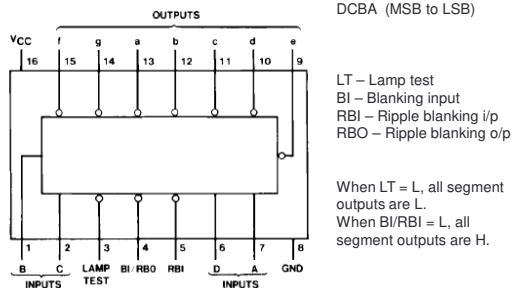

## FND 507

 

**Pin FND507 / 567**

- 1 Segment E
- 2 Segment D
- 3 Common Anode
- 4 Segment C
- 5 Decimal Point
- 6 Segment B
- 7 Segment A
- 8 Common Anode
- 9 Segment F
- 10 Segment G


## SYNC SEQUENTIAL LOGIC

Ch. 5

## Sequential Logic


- Combinational circuits - value of each output depends solely on the values of signals applied to the inputs.
- There exists another class of logic circuits in which the values of the outputs depend not only on the present values of the inputs but also on the past behavior of the circuit.
- Such circuits include storage elements that store the values of logic signals. The contents of the storage elements are said to represent the *state* of the circuit.

## Block diagram

 
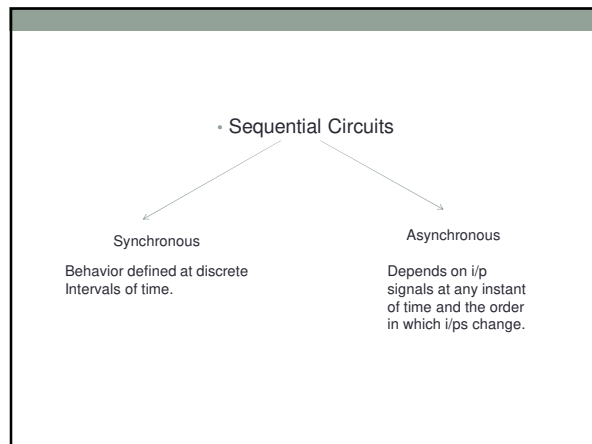
## Sequential Logic


- Sequential Logic – O/p are function not only of i/p but also of present state of storage elements.
- State of sequential ckt (at time  $t$ ) – Binary information stored in storage element at that time.
- Next state of storage elements is also function of input and present state.



## Synchronous sequential circuits

- Synchronous with the help of clock generator.
- Clock signal has periodic train of clock pulses.
- Storage elements are affected only with the arrival of each pulse.
- Activity within the circuit and the resulting updating of stored values is synchronized to the occurrence of clk pulses.
- **clocked sequential circuits**

## Block diagram

 

## STORAGE ELEMENTS

LATCHES


## Latches and Flip-flops

- *Storage elements that operate with signal levels (rather than signal transitions) are referred to as latches; those controlled by a clock transition are flip-flops.*
- Latches are said to be level sensitive devices; flip-flops are edge-sensitive devices.

## Latch

- a circuit which retains whatever output state results from a momentary input signal until reset by another signal.
- (of a device) become fixed in a particular state.

## S-R Latch

 

Function table


S	R	Q	Q'
1	0	1	0
0	0	1	0
0	0	0	1
1	1	0	0

After S=1, R=0

After S=0, R=1

Forbidden state

## SR Latch with NAND gates

 


S	R	Q	Q'
1	0	0	1
1	1	0	1
0	1	1	0
0	0	1	1

After S=1, R=0

After S=0, R=1


Forbidden state

## SR Latch with control input

 


En	S	R	Next state of Q
0	X	X	No change

## SR Latch with control input

 

En	S	R	Next state of Q
1	0	0	No change

## SR Latch with control input

 


En	S	R	Next state of Q
1	0	1	Q=0, Reset

- When  $En$  returns to 0, the circuit remains in its current state.
- The control input disables the circuit by applying 0 to  $En$ , so that the state of the output does not change regardless of the values of  $S$  and  $R$ .
- Moreover, when  $En = 1$  and both the  $S$  and  $R$  inputs are equal to 0, the state of the circuit does not change.


En	S	R	Next state
0	x	x	No change
1	0	0	No change
1	0	1	q=0 Reset
1	1	0	q=1 set
1	1	1	Indeterminate

## D Latch (Transparent Latch)

 

En	D	Next state
0	x	No change
1	0	Q=0 (Reset)
1	1	Q=1 (Set)


## Symbols

 


# FLIP-FLOPS
 
## Flip-flops

- Latches respond to the change in **level** of a clock pulse.
- State of the latches may keep changing for as long as the clock pulse stays at "active" level –Unreliable operation.
- Flip-flop is triggered only during a signal **transition** – providing proper operation in the sequential ckt having common clock.




## Edge-Triggered D Flip-Flop

 


A change in the output of the flip-flop can be triggered only by and during the transition of the clock from 1 to 0.

## Edge-Triggered D Flip-Flop

 - (1) the output may change only once,
- (2) a change in the output is triggered by the negative edge of the clock, and
- (3) the change may occur only during the clock's negative level.



## D Flip Flop

 


$$Q(t+1) = D$$

D Flip-Flop

D	Q(t + 1)	
0	0	Reset
1	1	Set

## J-K Flip Flop

 

JK Flip-Flop			
J	K	Q(t + 1)	
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement