
Name :

ID. No. :

Task: Design BCD adder using 4-bit binary adder IC 7483. You can use 2-input AND and 2-input OR gates other than 7483.