
Name :

ID. No. :

Task: Implement the following Boolean function only using 2-input NOR gates. Use minimum number gates. Draw logic diagram. Write truth table.

$$F(A,B,C,D) = \sum m(0, 1, 2, 3, 12, 13, 14, 15)$$