

# DIGITAL DESIGN

CS/ECE/EEE/INSTR F215

Sarang Dhongdi

## Example on MEV

**Ex 2:** Find the minimum Sum of Product form for function  $F_1$  and  $F_2$  using Variable Entered Mapping (VEM) technique. Assume D as Map Entered Variable (MEV).

| A | B | C | D | $F_1$ | $F_2$ |
|---|---|---|---|-------|-------|
| 0 | 0 | 0 | 0 | 0     | 1     |
| 0 | 0 | 0 | 1 | 0     | 1     |
| 0 | 0 | 1 | 0 | 1     | 1     |
| 0 | 0 | 1 | 1 | 1     | X     |
| 0 | 1 | 0 | 0 | X     | 1     |
| 0 | 1 | 0 | 1 | 0     | 0     |
| 0 | 1 | 1 | 0 | 1     | X     |
| 0 | 1 | 1 | 1 | 0     | 0     |
| 1 | 0 | 0 | 0 | 1     | 0     |
| 1 | 0 | 0 | 1 | 1     | 1     |
| 1 | 0 | 1 | 0 | 0     | 1     |
| 1 | 0 | 1 | 1 | 1     | 1     |
| 1 | 1 | 0 | 0 | X     | X     |
| 1 | 1 | 0 | 1 | 0     | X     |
| 1 | 1 | 1 | 0 | 0     | 0     |
| 1 | 1 | 1 | 1 | 0     | 0     |

## Example on MEV

**Ex 2:** Find the minimum Sum of Product form for function  $F_1$  and  $F_2$  using Variable Entered Mapping (VEM) technique. Assume D as Map Entered Variable (MEV).

| A | B | C | D | $F_1$ | $F_2$ |
|---|---|---|---|-------|-------|
| 0 | 0 | 0 | 0 | 0     | 1     |
| 0 | 0 | 0 | 1 | 0     | 1     |
| 0 | 0 | 1 | 0 | 1     | 1     |
| 0 | 0 | 1 | 1 | 1     | X     |
| 0 | 1 | 0 | 0 | X     | 1     |
| 0 | 1 | 0 | 1 | 0     | 0     |
| 0 | 1 | 1 | 0 | 1     | X     |
| 0 | 1 | 1 | 1 | 0     | 0     |
| 1 | 0 | 0 | 0 | 1     | 0     |
| 1 | 0 | 0 | 1 | 1     | 1     |
| 1 | 0 | 1 | 0 | 0     | 1     |
| 1 | 0 | 1 | 1 | 1     | 1     |
| 1 | 1 | 0 | 0 | X     | X     |
| 1 | 1 | 0 | 1 | 0     | X     |
| 1 | 1 | 1 | 0 | 0     | 0     |
| 1 | 1 | 1 | 1 | 0     | 0     |

0  
1  
D  
D  
1  
0  
D  
0

| BC | 00 | 01 | 11 | 10  |
|----|----|----|----|-----|
| A  |    |    |    |     |
| 0  | 0  | 1  | D' | D'φ |
| 1  | 1  | D  | 0  | D'φ |

| BC | 00   | 01   | 11 | 10  |
|----|------|------|----|-----|
| A  |      |      |    |     |
| 0  | 0    | D+D' | D' | D'φ |
| 1  | D+D' | D    | 0  | D'φ |

| BC | 00   | 01   | 11 | 10  |
|----|------|------|----|-----|
| A  |      |      |    |     |
| 0  | 0    | D+D' | D' | D'φ |
| 1  | D+D' | D    | 0  | D'φ |

## Step 2

- $MEV \rightarrow 0$
- $MEV' \rightarrow 0$
- $0 \rightarrow 0$
- $\phi \rightarrow \phi$
- $MEV, \phi \rightarrow 0$
- $MEV', \phi \rightarrow 0$
- $1 \rightarrow 1$  (If not completely covered)
- $1 \rightarrow \phi$  (If completely covered)
- $MEV+MEV' \phi \rightarrow 1$  (If not covered at all or only  $\phi$  covered)
- $MEV+MEV' \phi \rightarrow \phi$  (If completely covered or necessary terms are covered)
- Same for  $MEV'+MEV \phi$

| A \ BC |  | 00 | 01     | 11 | 10 |
|--------|--|----|--------|----|----|
|        |  |    |        |    |    |
| 0      |  | 0  | $\phi$ | 0  | 0  |
| 1      |  | 1  | 0      | 0  | 0  |

$A\bar{B}\bar{C}$

## Example on MEV

**Ex 2:** Find the minimum Sum of Product form for function  $F_1$  and  $F_2$  using Variable Entered Mapping (VEM) technique. Assume D as Map Entered Variable (MEV).

| A | B | C | D | $F_1$ | $F_2$ |
|---|---|---|---|-------|-------|
| 0 | 0 | 0 | 0 | 0     | 1     |
| 0 | 0 | 0 | 1 | 0     | 1     |
| 0 | 0 | 1 | 0 | 1     | 1     |
| 0 | 0 | 1 | 1 | 1     | X     |
| 0 | 1 | 0 | 0 | X     | 1     |
| 0 | 1 | 0 | 1 | 0     | 0     |
| 0 | 1 | 1 | 0 | 1     | X     |
| 0 | 1 | 1 | 1 | 0     | 0     |
| 1 | 0 | 0 | 0 | 1     | 0     |
| 1 | 0 | 0 | 1 | 1     | 1     |
| 1 | 0 | 1 | 0 | 0     | 1     |
| 1 | 0 | 1 | 1 | 1     | 1     |
| 1 | 1 | 0 | 0 | X     | X     |
| 1 | 1 | 0 | 1 | 0     | X     |
| 1 | 1 | 1 | 0 | 0     | 0     |
| 1 | 1 | 1 | 1 | 0     | 0     |

## Example on MEV

**Ex 2:** Find the minimum Sum of Product form for function  $F_1$  and  $F_2$  using Variable Entered Mapping (VEM) technique. Assume D as Map Entered Variable (MEV).

| A | B | C | D | $F_1$ | $F_2$ |
|---|---|---|---|-------|-------|
| 0 | 0 | 0 | 0 | 0     | 1     |
| 0 | 0 | 0 | 1 | 0     | 1     |
| 0 | 0 | 1 | 0 | 1     | 1     |
| 0 | 0 | 1 | 1 | 1     | X     |
| 0 | 1 | 0 | 0 | X     | 1     |
| 0 | 1 | 0 | 1 | 0     | 0     |
| 0 | 1 | 1 | 0 | 1     | X     |
| 0 | 1 | 1 | 1 | 0     | 0     |
| 1 | 0 | 0 | 0 | 1     | 0     |
| 1 | 0 | 0 | 1 | 1     | 1     |
| 1 | 0 | 1 | 0 | 0     | 1     |
| 1 | 0 | 1 | 1 | 1     | 1     |
| 1 | 1 | 0 | 0 | X     | X     |
| 1 | 1 | 0 | 1 | 0     | X     |
| 1 | 1 | 1 | 0 | 0     | 0     |
| 1 | 1 | 1 | 1 | 0     | 0     |

| A \ BC |  | 00 | 01         | 11       | 10     |
|--------|--|----|------------|----------|--------|
|        |  |    |            |          |        |
| 0      |  | 1  | $D'+D\phi$ | $D'\phi$ | $D'$   |
| 1      |  | D  | 1          | 0        | $\phi$ |

| A \ BC |  | 00     | 01         | 11       | 10     |
|--------|--|--------|------------|----------|--------|
|        |  |        |            |          |        |
| 0      |  | $D+D'$ | $D'+D\phi$ | $D'\phi$ | $D'$   |
| 1      |  | D      | $D+D'$     | 0        | $\phi$ |

| A \ BC | 00     | 01        | 11       | 10     |
|--------|--------|-----------|----------|--------|
| 0      | $D+D'$ | $D+D\phi$ | $D'\phi$ | $D'$   |
| 1      | $D$    | $D+D'$    | $0$      | $\phi$ |

$\bar{A}\bar{B}$

| A \ BC | 00     | 01         | 11       | 10     |
|--------|--------|------------|----------|--------|
| 0      | $D+D'$ | $D'+D\phi$ | $D'\phi$ | $D'$   |
| 1      | $D$    | $D+D'$     | $0$      | $\phi$ |

$\bar{B}D$

| A \ BC | 00     | 01     | 11  | 10     |
|--------|--------|--------|-----|--------|
| 0      | $\phi$ | $\phi$ | $0$ | $0$    |
| 1      | $0$    | $1$    | $0$ | $\phi$ |

| A \ BC | 00     | 01     | 11  | 10     |
|--------|--------|--------|-----|--------|
| 0      | $\phi$ | $\phi$ | $0$ | $0$    |
| 1      | $0$    | $1$    | $0$ | $\phi$ |

$\bar{B}C$

## TWO LEVEL IMPLEMENTATION

### Two level implementations

- 4 types of gates – AND, OR, NAND, NOR
- Use 1 type of gate for level 1 and one type for level 2.
- Same type can be used for level 2.
- Total 16 combinations.
- 8 combinations – degenerate form
- Remaining 8 – Non-degenerate form

## Two level implementations

- Degenerate
  - AND-AND
  - OR-OR
  - AND-NAND
  - OR-NOR
  - NAND-NOR
  - NAND-OR
  - NOR-NAND
  - NOR-AND
- Nondegenerate
  - AND-OR
  - NAND-NAND
  - OR-AND
  - NOR-NOR
  - NOR-OR
  - NAND-AND
  - OR-NAND
  - AND-NOR

## AND-OR-INVERT (AND-NOR)


| yz \ x | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 1  | 0  | 0  | 0  |
| 1      | 0  | 0  | 0  | 1  |

Combine 0's to obtain complement of function in SOP form


$$F' = z + xy' + x'y$$

$$F = (z + xy' + x'y)'$$

$$F = (z + xy' + x'y)'$$

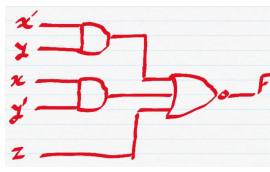

NAND-AND

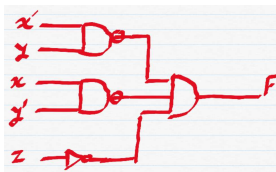

## OR-AND-INVERT (OR-NAND)

| yz \ x | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0      | 1  | 0  | 0  | 0  |
| 1      | 0  | 0  | 0  | 1  |


Combine 1's for function F, then take complement of function in POS form

$$F = x'y'z' + xyz'$$


$$F' = (x'y'z' + xyz')' = (x+y+z)(x'+y'+z)$$

$$F = [(x+y+z)(x'+y'+z)]'$$

$$F = [(x+y+z)(x'+y'+z)]'$$

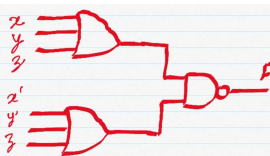

NOR-OR

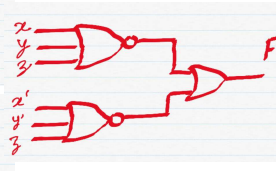

## Exclusive-OR function


XOR



| A | B | F = A.B' + A'B<br>F = A ⊕ B |
|---|---|-----------------------------|
| 0 | 0 | 0                           |
| 0 | 1 | 1                           |
| 1 | 0 | 1                           |
| 1 | 1 | 0                           |


- $A \oplus 0 = A$
- $A \oplus 1 = A'$
- $A \oplus A = 0$
- $A \oplus A' = 1$
- $A \oplus B' = A' \oplus B = (A \oplus B)'$

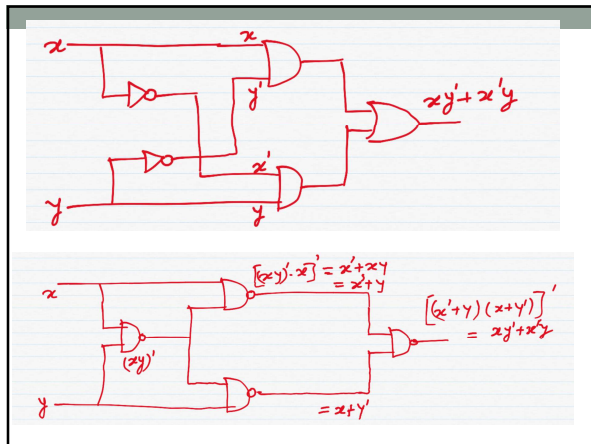- Ex-OR  $A \oplus B = AB' + A'B$
- Ex-NOR  $(A \oplus B)' = (AB' + A'B)'$
- $= (A' + B)(A + B')$
- $= AB + A'B'$
- $(A \oplus B) \oplus C =$
- $= A \oplus (B \oplus C)$
- $= A \oplus B \oplus C$


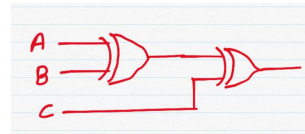
## Exclusive-OR function

- For three inputs,
- $F = A \oplus B \oplus C = (AB' + A'B)C' + (AB + A'B')C$
- $= AB'C' + A'BC' + ABC + A'B'C$
- $= \sum (1, 2, 4, 7)$



| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

## Odd and Even function

| BC | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| A  | 0  |    | 1  |    |
| 0  |    | 1  |    | 1  |
| 1  | 1  |    | 1  |    |
| 10 |    |    |    | 1  |


| BC | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| A  | 0  | 1  |    | 1  |
| 0  | 1  |    | 1  |    |
| 1  |    | 1  |    | 1  |
| 10 |    |    |    | 1  |

## Four variable Ex-OR

| CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| AB | 00 |    | 1  |    |
| 00 |    | 1  |    | 1  |
| 01 | 1  |    | 1  |    |
| 11 |    | 1  |    | 1  |
| 10 | 1  |    | 1  |    |

## Parity Generation and Checking

| Message Bits | Parity Bit |
|--------------|------------|
| A B C        | P          |
| 0 0 0        | 0          |
| 0 0 1        | 1          |
| 0 1 0        | 1          |
| 0 1 1        | 0          |
| 1 0 0        | 1          |
| 1 0 1        | 0          |
| 1 1 0        | 0          |
| 1 1 1        | 1          |

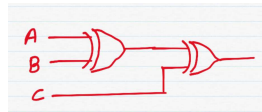


## Parity Generation and Checking

| Received bits | Parity Error Check |
|---------------|--------------------|
| A B C P       | F                  |
| 0 0 0 0       | 0                  |
| 0 0 1 1       | 0                  |
| 0 1 0 1       | 0                  |
| 0 1 1 0       | 0                  |
| 1 0 0 1       | 0                  |
| 1 0 1 0       | 0                  |
| 1 1 0 0       | 0                  |
| 1 1 1 1       | 0                  |


| Received bits | Parity Error Check |
|---------------|--------------------|
| A B C P       | F                  |
| 0 0 0 1       | 1                  |
| 0 0 1 0       | 1                  |
| 0 1 0 0       | 1                  |
| 0 1 1 1       | 1                  |
| 1 0 0 0       | 1                  |
| 1 0 1 1       | 1                  |
| 1 1 0 1       | 1                  |
| 1 1 1 0       | 1                  |

### Four variable Ex-OR

| AB \ CP | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      |    | 1  |    | 1  |
| 01      | 1  |    | 1  |    |
| 11      |    | 1  |    | 1  |
| 10      | 1  |    | 1  |    |

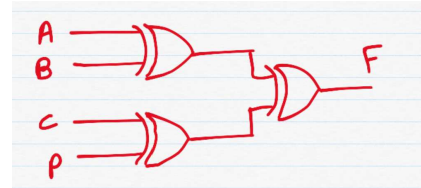

## COMBINATIONAL CIRCUITS

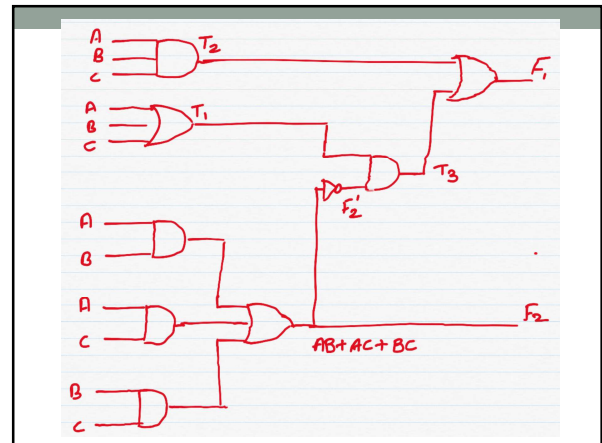

- $F1 = T_3 + T_2$
- $= F_2' T_1 + ABC$
- $= (AB + AC + BC)'(A + B + C) + ABC$
- $= A'BC' + A'B'C + AB'C' + ABC$

### Truthtable

| A | B | C | F2 | F2' | T1 | T2 | T3 | F1 |
|---|---|---|----|-----|----|----|----|----|
| 0 | 0 | 0 | 0  | 1   | 0  | 0  | 0  | 0  |
| 0 | 0 | 1 | 0  | 1   | 1  | 0  | 1  | 1  |
| 0 | 1 | 0 | 0  | 1   | 1  | 0  | 1  | 1  |
| 0 | 1 | 1 | 1  | 0   | 1  | 0  | 0  | 0  |
| 1 | 0 | 0 | 0  | 1   | 1  | 0  | 1  | 1  |
| 1 | 0 | 1 | 1  | 0   | 1  | 0  | 0  | 0  |
| 1 | 1 | 0 | 1  | 0   | 1  | 0  | 0  | 0  |
| 1 | 1 | 1 | 1  | 0   | 1  | 1  | 0  | 1  |



# BINARY ADDER AND SUBTRACTOR

## Half Adder

| X | Y | C | S |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

$$S = x'y + xy'$$

$$C = xy$$

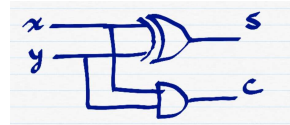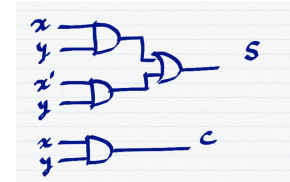


## Full Adder

$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$


| X | Y | Z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

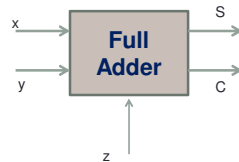

## Full Adder


$$S = x'y'z + x'yz' + xy'z' + xyz$$

$$C = xy + xz + yz$$

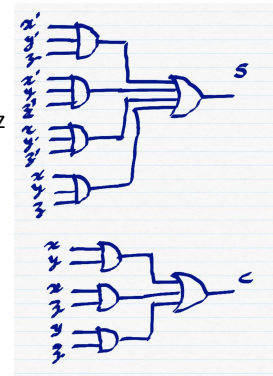

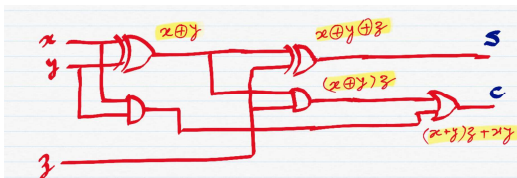
## Circuit implementation

- $S = x \oplus y \oplus z$
- $C = xy + xz + yz$
- $C = xy + z(x \oplus y)$


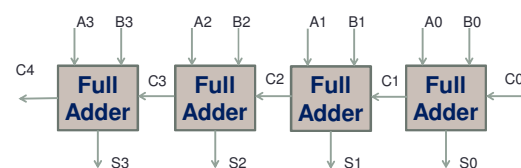
## Binary adder

- Add two 4 – bit nos.
- Augend - A3A2A1A0
- Addend – B3B2B1B0



## Carry Propagation

- For a "Carry Lookahead logic",
- we define two new variables,


$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$G_i$  = carry generator  
 $P_i$  = Carry Propagate



$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

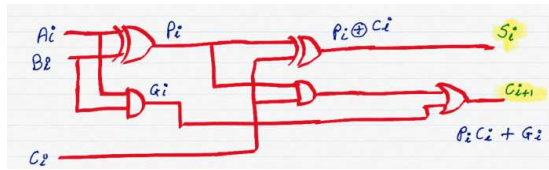
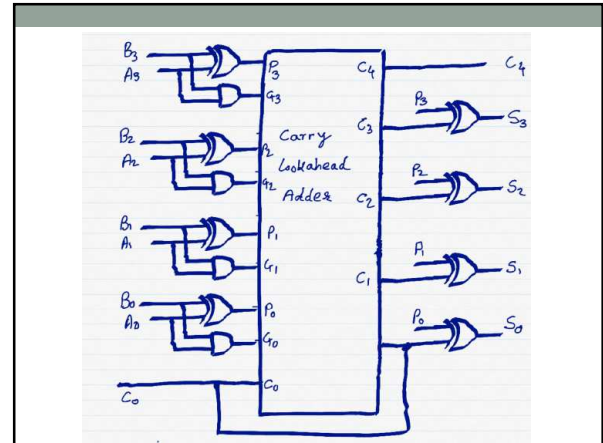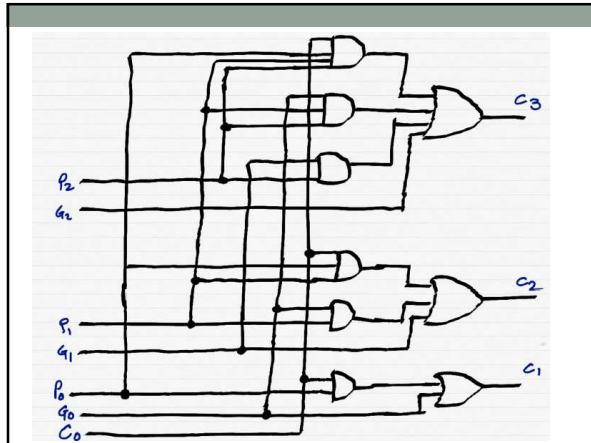
## Carry lookahead logic

- $C_0$  = Input carry
- $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 C_1$ 
  - $= G_1 + P_1(G_0 + P_0 C_0)$
  - $= G_1 + P_1 G_0 + P_1 P_0 C_0$
- $C_3 = G_2 + P_2 C_2$ 
  - $= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$





## Half Subtractor

| X | Y | D | B |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

$$D = x'y + xy'$$

$$B = x'y$$

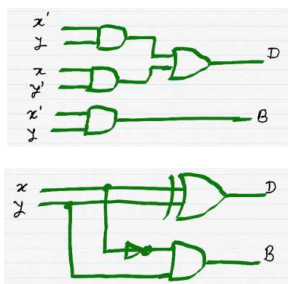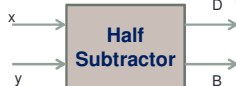


## Full Subtractor





$$D = x'y'z + x'yz' + xy'z' + xyz$$

$$B = x'z + x'y + yz$$

| X | Y | Z | D | B |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

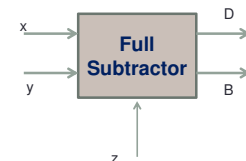



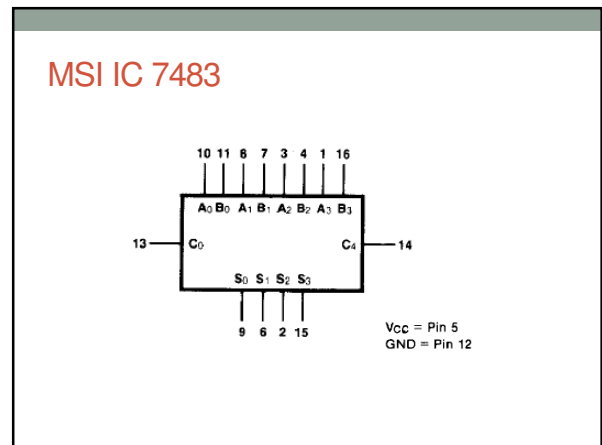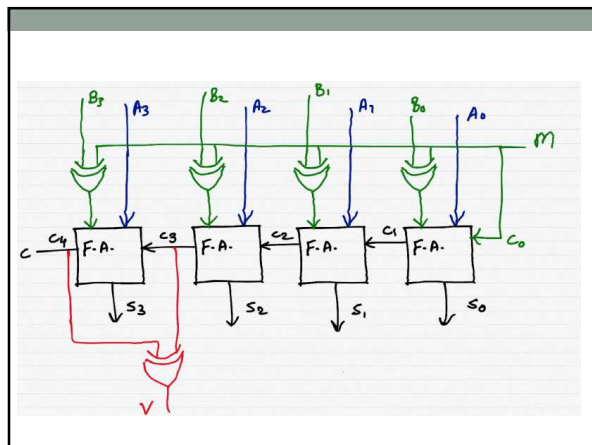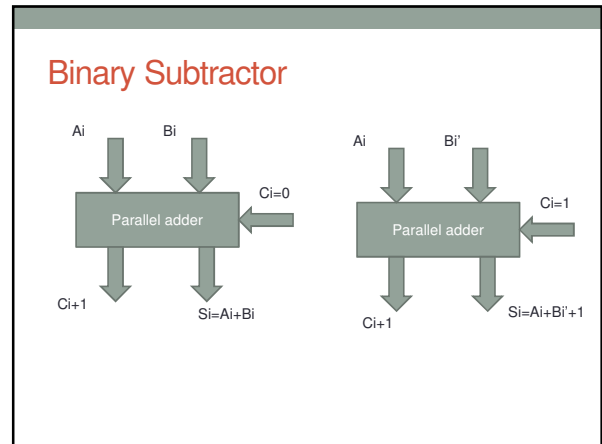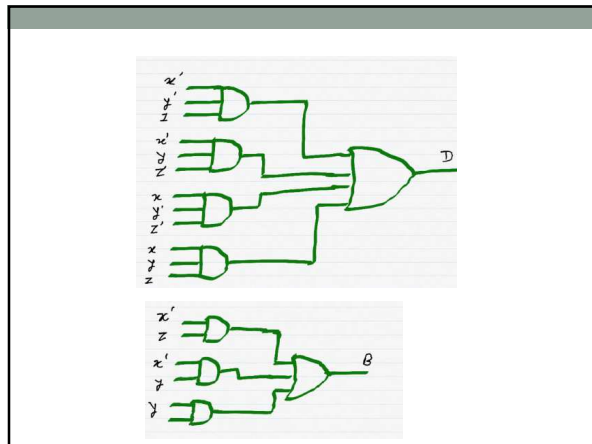


### BCD Adder

| No. | Binary sum |    |    |    |    | BCD sum |    |    |    |    |
|-----|------------|----|----|----|----|---------|----|----|----|----|
|     | K          | Z8 | Z4 | Z2 | Z1 | C       | S8 | S4 | S2 | S1 |
| 0   | 0          | 0  | 0  | 0  | 0  | 0       | 0  | 0  | 0  | 0  |
| 1   | 0          | 0  | 0  | 0  | 1  | 0       | 0  | 0  | 0  | 1  |
| 2   | 0          | 0  | 0  | 1  | 0  | 0       | 0  | 0  | 1  | 0  |
| 3   | 0          | 0  | 0  | 1  | 1  | 0       | 0  | 0  | 1  | 1  |
| 4   | 0          | 0  | 1  | 0  | 0  | 0       | 0  | 1  | 0  | 0  |
| 5   | 0          | 0  | 1  | 0  | 1  | 0       | 0  | 1  | 0  | 1  |
| 6   | 0          | 0  | 1  | 1  | 0  | 0       | 0  | 1  | 1  | 0  |
| 7   | 0          | 0  | 1  | 1  | 1  | 0       | 0  | 1  | 1  | 1  |
| 8   | 0          | 1  | 0  | 0  | 0  | 0       | 1  | 0  | 0  | 0  |
| 9   | 0          | 1  | 0  | 0  | 1  | 0       | 1  | 0  | 0  | 1  |

### BCD Adder

| No. | Binary sum |    |    |    |    | BCD sum |    |    |    |    |
|-----|------------|----|----|----|----|---------|----|----|----|----|
|     | K          | Z8 | Z4 | Z2 | Z1 | C       | S8 | S4 | S2 | S1 |
| 10  | 0          | 1  | 0  | 1  | 0  | 1       | 0  | 0  | 0  | 0  |
| 11  | 0          | 1  | 0  | 1  | 1  | 1       | 0  | 0  | 0  | 1  |
| 12  | 0          | 1  | 1  | 0  | 0  | 1       | 0  | 0  | 1  | 0  |
| 13  | 0          | 1  | 1  | 0  | 1  | 1       | 0  | 0  | 1  | 1  |
| 14  | 0          | 1  | 1  | 1  | 0  | 1       | 0  | 1  | 0  | 0  |
| 15  | 0          | 1  | 1  | 1  | 1  | 1       | 0  | 1  | 0  | 1  |
| 16  | 1          | 0  | 0  | 0  | 0  | 1       | 0  | 1  | 1  | 0  |
| 17  | 1          | 0  | 0  | 0  | 1  | 1       | 0  | 1  | 1  | 1  |
| 18  | 1          | 0  | 0  | 1  | 0  | 1       | 1  | 0  | 0  | 0  |
| 19  | 1          | 0  | 0  | 1  | 1  | 1       | 1  | 0  | 0  | 1  |

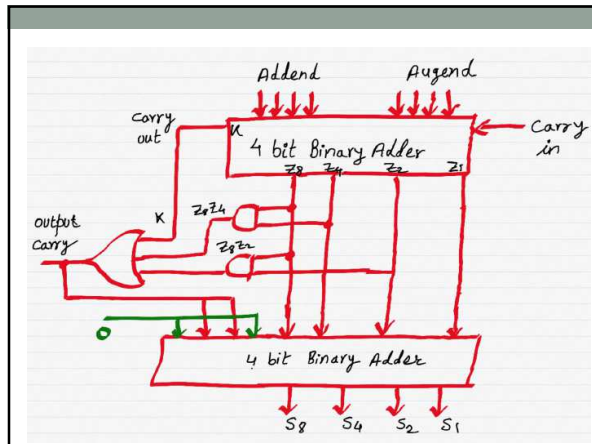

## Binary Multiplier


- Multiplication of two 2-bit numbers
- Multiplicand B1B0
- Multiplier A1A0
- - Solve using k-map (and minimum gate implementation)
- - Implement using adders

| Inputs |    |    |    | Outputs |    |    |    |
|--------|----|----|----|---------|----|----|----|
| A1     | A0 | B1 | B0 | P3      | P2 | P1 | P0 |
| 0      | 0  | 0  | 0  | 0       | 0  | 0  | 0  |
| 0      | 0  | 0  | 1  | 0       | 0  | 0  | 0  |
| 0      | 0  | 1  | 0  | 0       | 0  | 0  | 0  |
| 0      | 0  | 1  | 1  | 0       | 0  | 0  | 0  |
| 0      | 1  | 0  | 0  | 0       | 0  | 0  | 0  |
| 0      | 1  | 0  | 1  | 0       | 0  | 0  | 1  |
| 0      | 1  | 1  | 0  | 0       | 0  | 1  | 0  |
| 0      | 1  | 1  | 1  | 0       | 0  | 1  | 1  |
| 1      | 0  | 0  | 0  | 0       | 0  | 0  | 0  |
| 1      | 0  | 0  | 1  | 0       | 0  | 1  | 0  |
| 1      | 0  | 1  | 1  | 0       | 1  | 1  | 0  |
| 1      | 1  | 0  | 0  | 0       | 0  | 0  | 0  |
| 1      | 1  | 0  | 1  | 0       | 0  | 1  | 1  |
| 1      | 1  | 1  | 0  | 0       | 1  | 1  | 0  |
| 1      | 1  | 1  | 1  | 1       | 0  | 0  | 1  |


## Equations


- $P3 = F(A1, A0, B1, B0) = \sum (15)$
- $P2 = F(A1, A0, B1, B0) = \sum (10, 11, 14)$
- $P1 = F(A1, A0, B1, B0) = \sum (6, 7, 9, 11, 13, 14)$
- $P0 = F(A1, A0, B1, B0) = \sum (5, 7, 13, 15)$
- $P3 = A1A0B1B0$
- $P2 = A1A0'B1 + A1B1B0' = A1B1(A0B0)'$
- $P1 = A1'A0B1 + A0B1B0' + A1B1'B0 + A1A0'B0 =$   
 $= A0B1(A1B0)' + A1B0(B1A0)'$
- $P0 = A0B0$

## Implementation

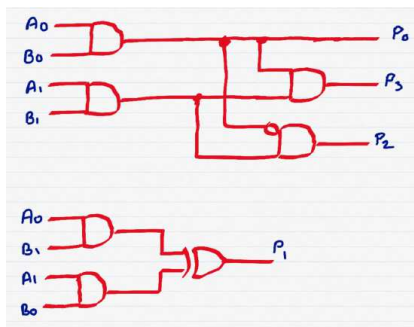

## Implementation using Adders

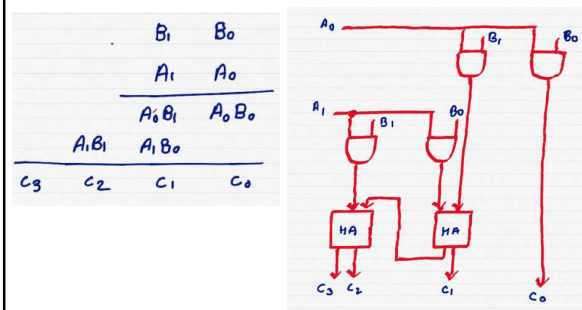

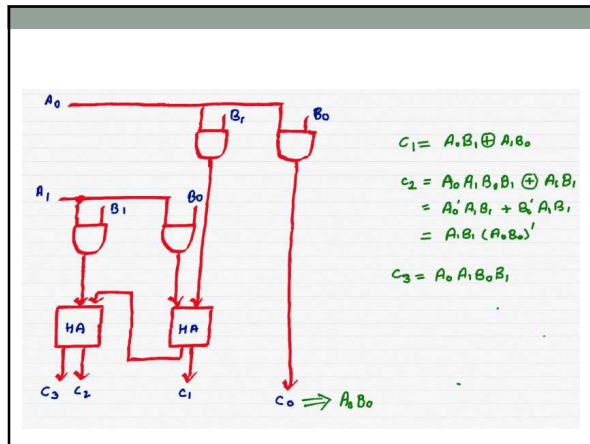

### Multiplication of 4 bit by 3 bit

$$\begin{array}{r}
 B_3 \ B_2 \ B_1 \ B_0 \\
 \times \quad A_3 \ A_2 \ A_1 \ A_0 \\
 \hline
 A_0B_3 \ A_0B_2 \ A_0B_1 \ A_0B_0 \\
 A_1B_3 \ A_1B_2 \ A_1B_1 \ A_1B_0 \\
 A_2B_3 \ A_2B_2 \ A_2B_1 \ A_2B_0 \\
 A_3B_3 \ A_3B_2 \ A_3B_1 \ A_3B_0
 \end{array}$$

