

DIGITAL DESIGN

CS/ECE/EEE/INSTR F215


Sarang Dhongdi

DECODER

Decoder

- n inputs \rightarrow (max) 2^n unique output lines
- n -to- m line decoder ($m \leq 2^n$)
- Generates minterms of n input variables
- General decoders
 - 2 to 4 line decoder
 - 3 to 8 line decoder
 - 4 to 16 line decoder


Two-to-Four line Decoder

 


Three-to-Eight line decoder

Inputs			Outputs							
X	Y	Z	D0	D1	D2	D3	D4	D5	D6	D7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Implement Full adder using 3:8 decoder

 


2-to-4 line Decoder with Enable input

 


2-to-4 line Decoder with Enable input


Inputs			Outputs			
E	A	B	D0	D1	D2	D3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

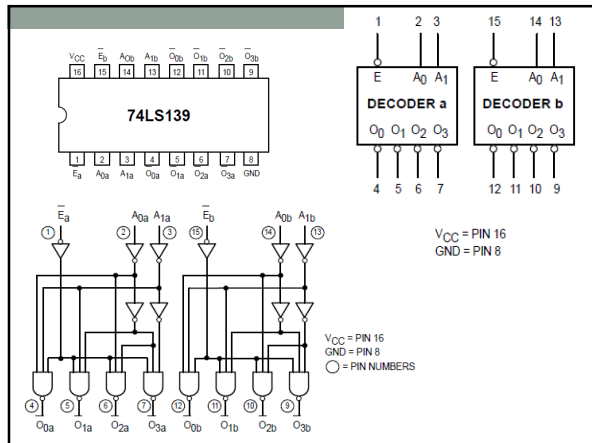

 
Implement Full adder using 3:8 decoder, with enable i/p




3:8 decoder – MSI IC 74138

 

Decoder-Demultiplexer

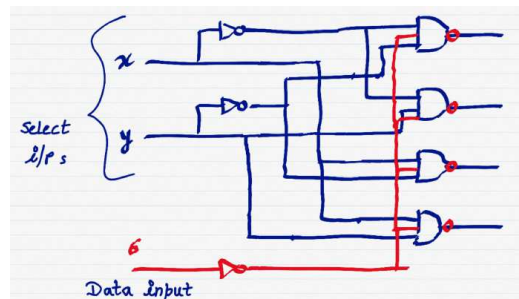

3:8 decoder – MSI IC 74138

 

Truthtable from Datasheet

INPUTS					OUTPUTS							
ENABLE		SELECT										
G1	G2*	C	B	A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X	H	X	X	X	H	H	H	H	H	H	H	H
L	X	X	X	X	H	H	H	H	H	H	H	H
H	L	L	L	L	L	H	H	H	H	H	H	H
H	L	L	L	H	H	L	H	H	H	H	H	H
H	L	L	H	L	H	H	L	H	H	H	H	H
H	L	L	H	H	H	H	L	H	H	H	H	H
H	L	H	L	L	H	H	H	L	H	H	H	H
H	L	H	L	H	H	H	H	L	H	H	H	H
H	L	H	H	L	H	H	H	H	L	H	H	H
H	L	H	H	H	H	H	H	H	H	L	H	H

Encoders

- Inverse operation of that of Decoders
- 2^n input lines \rightarrow n output lines
- Output is binary code of the input

Octal-to-Binary Encoder

- Assumption – only one i/p has value 1 at any given time.

Inputs								Outputs			
D0	D1	D2	D3	D4	D5	D6	D7	X	Y	Z	
1	0	0	0	0	0	0	0	0	0	0	$Z = D1 + D3 + D5 + D7$
0	1	0	0	0	0	0	0	0	0	1	$Y = D2 + D3 + D6 + D7$
0	0	1	0	0	0	0	0	0	1	0	$X = D4 + D5 + D6 + D7$
0	0	0	1	0	0	0	0	0	1	1	Issues – • When 2 i/ps are simultaneously 1. • When none of the i/p is 1, o/p is 0
0	0	0	0	1	0	0	0	1	0	0	
0	0	0	0	0	1	0	0	1	0	1	
0	0	0	0	0	0	1	0	1	1	0	
0	0	0	0	0	0	0	1	1	1	1	

Priority Encoder

- If two or more inputs are equal to 1 at the same time, the input having highest priority will take precedence.

Inputs				Outputs		
D0	D1	D2	D3	A	B	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

Maps for Priority Encoders

• A = ?

		D2D3			
D0D1		00	01	11	10
		X	1	1	1
01			1	1	1
11			1	1	1
10			1	1	1

Maps for Priority Encoders

• $A = D_2 + D_3$

D ₀ D ₁ \ D ₂ D ₃	00	01	11	10
00	X	1	1	1
01		1	1	1
11		1	1	1
10		1	1	1

Maps for Priority Encoders

• $B = ?$

D ₀ D ₁ \ D ₂ D ₃	00	01	11	10
00	X	1	1	
01	1	1	1	
11	1	1	1	
10		1	1	


Maps for Priority Encoders

• $B = D_3 + D_1 D_2'$


D ₀ D ₁ \ D ₂ D ₃	00	01	11	10
00	X	1	1	
01	1	1	1	
11	1	1	1	
10		1	1	

Four input Priority Encoder

 - $A = D_2 + D_3$
- $B = D_3 + D_1 D_2'$
- $V = D_0 + D_1 + D_2 + D_3$




Multiplexer

 

Multiplexer

- Selects 'binary' information from one of the many i/p lines and connects it to a single o/p line.
- 2^n i/p lines, n selection lines
- Combination of select lines determines which i/p is selected.
- Also known as "Data selector"

Four-to-One line multiplexer

 


Mux MSI IC's

- 74153 – Dual 4:1 Mux
- 74151 – 8:1 Mux
- 74150 – 16:1 Mux

Boolean function implementation


$$f(x,y,z) = \sum (1,2,6,7)$$

 

$$f(A,B,C,D) = \sum (1,3,4,11,12,13,14,15)$$

A	B	C	D	O/p
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

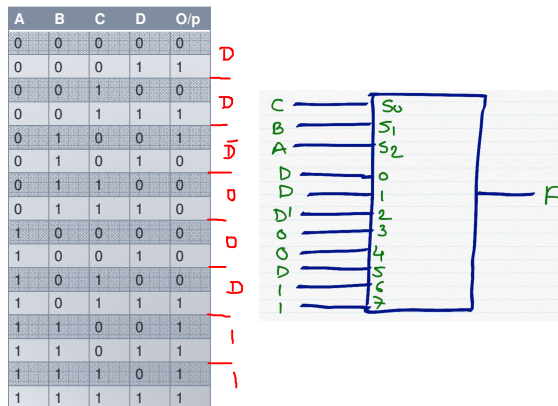
$$f(A,B,C,D) = \sum (1,3,4,11,12,13,14,15)$$



Three-State Gates

- Third-state is high-impedance state –
- A) logic behaves like an open ckt, i.e. o/p is disconnected
- B) Ckt has no logic significance
- C) Ckt connected to the output of the three-state gate is not affected by the inputs.

Three-State Gate -Buffer

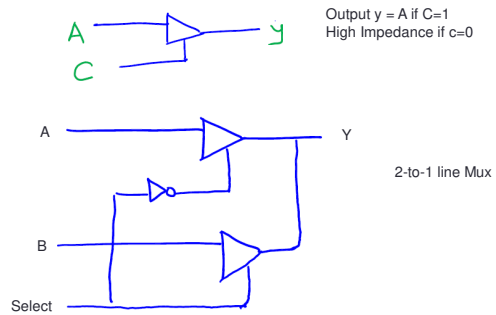

4-to-1 line Mux

